

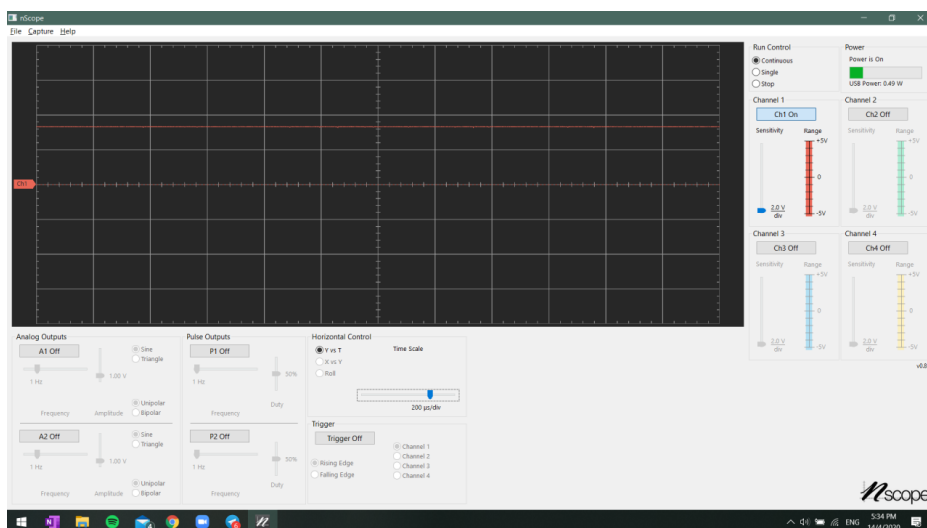


Building and testing the 3.3V regulator

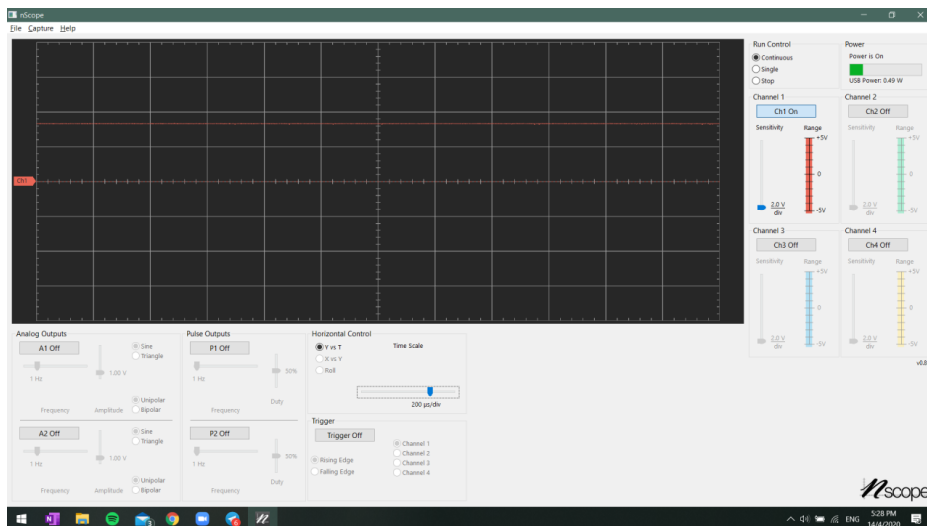

I didn't get any noise throughout but I added the capacitors anyway.

Building the circuit

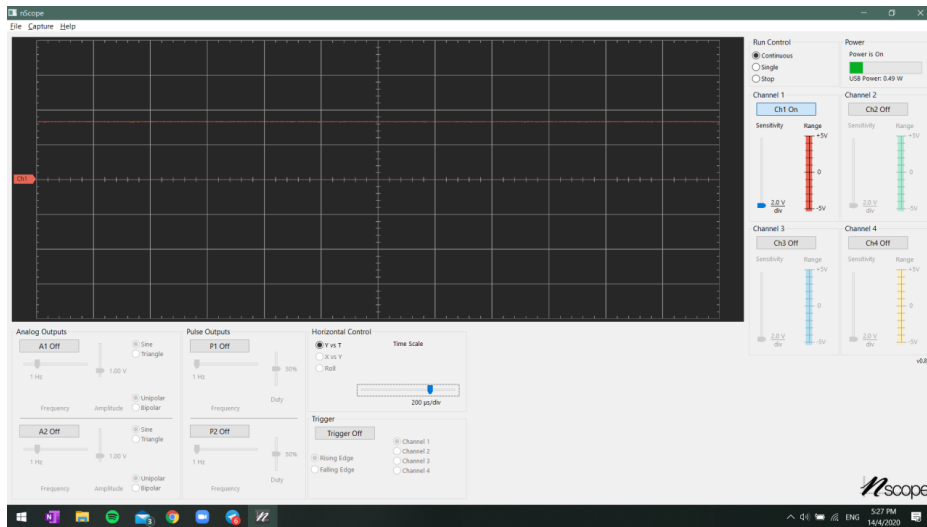